

LECTURE 230 – DESIGN OF TWO-STAGE OP AMPS

LECTURE OUTLINE

Outline

- Steps in Designing an Op Amp
- Design Procedure for a Two-Stage Op Amp
- Design Example of a Two-Stage Op Amp
- Right Half Plane Zero
- PSRR of the Two-Stage Op Amp
- Summary

CMOS Analog Circuit Design, 2nd Edition Reference

Pages 269-293

STEPS IN DESIGNING A CMOS OP AMP

Steps

- 1.) Choosing or creating the basic structure of the op amp.
This step results in a schematic showing the transistors and their interconnections.
This diagram does not change throughout the remainder of the design unless the specifications cannot be met, then a new or modified structure must be developed.
- 2.) Selection of the dc currents and transistor sizes.
Most of the effort of design is in this category.
Simulators are used to aid the designer in this phase.
- 3.) Physical implementation of the design.
Layout of the transistors
Floorplanning the connections, pin-outs, power supply buses and grounds
Extraction of the physical parasitics and re-simulation
Verification that the layout is a physical representation of the circuit.
- 4.) Fabrication
- 5.) Measurement
Verification of the specifications
Modification of the design as necessary

Design Inputs

Boundary conditions:

1. Process specification (V_T , K' , C_{ox} , etc.)
2. Supply voltage and range
3. Supply current and range
4. Operating temperature and range


Requirements:

1. Gain
2. Gain bandwidth
3. Settling time
4. Slew rate
5. Common-mode input range, $ICMR$
6. Common-mode rejection ratio, $CMRR$
7. Power-supply rejection ratio, $PSRR$
8. Output-voltage swing
9. Output resistance
10. Offset
11. Noise
12. Layout area

Outputs of Op Amp Design

The basic outputs of design are:

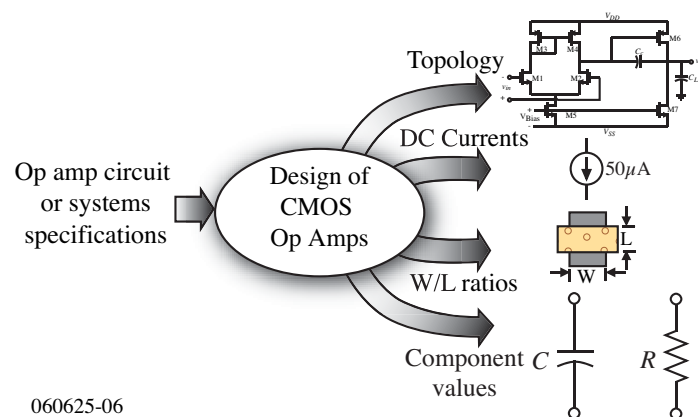- 1.) The topology
- 2.) The dc currents
- 3.) The W and L values of transistors
- 4.) The values of components



Some Practical Thoughts on Op Amp Design

- 1.) Decide upon a suitable topology.
 - Experience is a great help
 - The topology should be the one capable of meeting most of the specifications
 - Try to avoid “inventing” a new topology but start with an existing topology
- 2.) Determine the type of compensation needed to meet the specifications.
 - Consider the load and stability requirements
 - Use some form of Miller compensation or a self-compensated approach
- 3.) Design dc currents and device sizes for proper dc, ac, and transient performance.
 - This begins with hand calculations based upon approximate design equations.
 - Compensation components are also sized in this step of the procedure.
 - After each device is sized by hand, a circuit simulator is used to fine tune the design

Two basic steps of design:

- 1.) “First-cut” - this step is to use hand calculations to propose a design that has potential of satisfying the specifications. Design robustness is developed in this step.
- 2.) Optimization - this step uses the computer to refine and optimize the design.

A DESIGN PROCEDURE FOR THE TWO-STAGE CMOS OP AMP

Unbuffered, Two-Stage CMOS Op Amp

 


Fig. 6.3-1

Notation:

$$S_i = \frac{W_i}{L_i} = W/L \text{ of the } i\text{th transistor}$$

DC Balance Conditions for the Two-Stage Op Amp

For best performance, keep all transistors in saturation.

M4 is the only transistor that cannot be forced into saturation by internal connections or external voltages.

Therefore, we develop conditions to force M4 to be in saturation.

1.) First *assume* that $V_{SG4} = V_{SG6}$. This will cause “proper mirroring” in the M3-M4 mirror. Also, the gate and drain of M4 are at the same potential so that M4 is “guaranteed” to be in saturation.

2.) If $V_{SG4} = V_{SG6}$, then $I_6 = \left(\frac{S_6}{S_4}\right)I_4$

3.) However, $I_7 = \left(\frac{S_7}{S_5}\right)I_5 = \left(\frac{S_7}{S_5}\right)(2I_4)$

4.) For balance, I_6 must equal $I_7 \Rightarrow \boxed{\frac{S_6}{S_4} = \frac{2S_7}{S_5}}$ called the “balance conditions”

5.) So if the balance conditions are satisfied, then $V_{DG4} = 0$ and M4 is saturated.

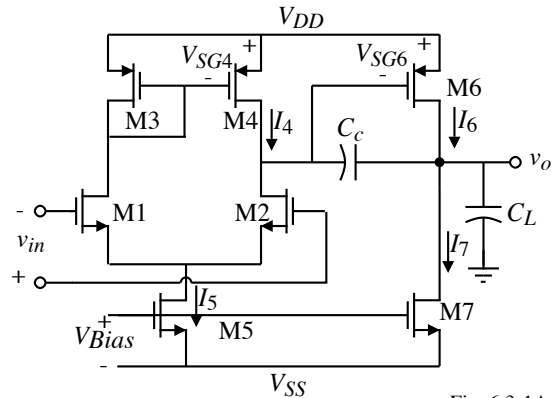


Fig. 6.3-1A

Summary of the Design Relationships for the Two-Stage Op Amp

$$\text{Slew rate } SR = \frac{I_5}{C_c} \text{ (Assuming } I_7 \gg I_5 \text{ and } C_L > C_c)$$

$$\text{First-stage gain } A_{v1} = \frac{g_{m1}}{g_{ds2} + g_{ds4}} = \frac{2g_{m1}}{I_5(l_2 + l_4)}$$

$$\text{Second-stage gain } A_{v2} = \frac{g_{m6}}{g_{ds6} + g_{ds7}} = \frac{g_{m6}}{I_6(l_6 + l_7)}$$

$$\text{Gain-bandwidth } GB = \frac{g_{m1}}{C_c}$$

$$\text{Output pole } p_2 = \frac{-g_{m6}}{C_L}$$

$$\text{RHP zero } z_1 = \frac{g_{m6}}{C_c}$$

60° phase margin requires that $g_{m6} = 2.2g_{m2}(C_L/C_c)$ if all other roots are $\geq 10GB$.

$$\text{Positive ICMR } V_{in(max)} = V_{DD} - \sqrt{\frac{I_5}{b_3}} - |V_{T03}|_{(max)} + V_{T1(min)}$$

$$\text{Negative ICMR } V_{in(min)} = V_{SS} + \sqrt{\frac{I_5}{b_1}} + V_{T1(max)} + V_{DS5(sat)}$$

Op Amp Specifications

The following design procedure assumes that specifications for the following parameters are given.

1. Gain at dc, $A_v(0)$
2. Gain-bandwidth, GB
3. Phase margin (or settling time)
4. Input common-mode range, ICMR
5. Load Capacitance, C_L
6. Slew-rate, SR
7. Output voltage swing
8. Power dissipation, P_{diss}

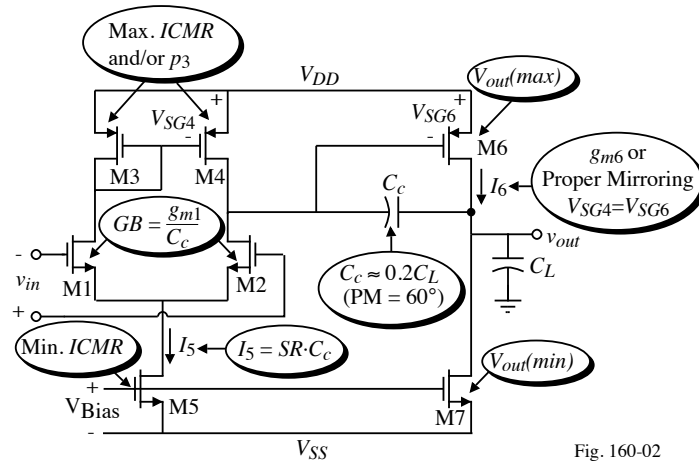


Fig. 160-02

Unbuffered Op Amp Design Procedure

This design procedure assumes that the gain at dc (A_v), unity gain bandwidth (GB), input common mode range ($V_{in(min)}$ and $V_{in(max)}$), load capacitance (C_L), slew rate (SR), settling time (T_s), output voltage swing ($V_{out(max)}$ and $V_{out(min)}$), and power dissipation (P_{diss}) are given. Choose the smallest device length which will keep the channel modulation parameter constant and give good matching for current mirrors.

1. From the desired phase margin, choose the minimum value for C_c , i.e. for a 60° phase margin we use the following relationship. This assumes that $z \geq 10GB$.

$$C_c > 0.22C_L$$

2. Determine the minimum value for the “tail current” (I_5) from

$$I_5 = SR \cdot C_c$$

3. Design for S_3 from the maximum input voltage specification.

$$S_3 = \frac{I_5}{K'_3[V_{DD} - V_{in(max)} - |V_{T03}|(max) + V_{T1}(min)]^2}$$

4. Verify that the pole of M3 due to C_{gs3} and C_{gs4} ($= 0.67W_3L_3C_{ox}$) will not be dominant by assuming it to be greater than $10GB$

$$\frac{gm_3}{2C_{gs3}} > 10GB.$$

Unbuffered Op Amp Design Procedure - Continued

5. Design for S_1 (S_2) to achieve the desired GB .

$$g_{m1} = GB \cdot C_c \rightarrow S_2 = \frac{g_{m1}^2}{K'_1 I_5}$$

6. Design for S_5 from the minimum input voltage. First calculate $V_{DS5}(\text{sat})$ then find S_5 .

$$V_{DS5}(\text{sat}) = V_{in}(\text{min}) - V_{SS} - \sqrt{\frac{I_5}{\beta_1}} - V_{T1}(\text{max}) \geq 100 \text{ mV} \rightarrow S_5 = \frac{2I_5}{K'_5 [V_{DS5}(\text{sat})]^2}$$

7. Find S_6 by letting the second pole (p_2) be equal to 2.2 times GB and assuming that $V_{SG4} = V_{SG6}$.

$$g_{m6} = 2.2g_{m2}(C_L/C_c) \quad \text{and} \quad \frac{g_{m6}}{g_{m4}} = \frac{\sqrt{2K_P S_6 I_6}}{\sqrt{2K_P S_4 I_4}} = \sqrt{\frac{S_6 I_6}{S_4 I_4}} = \frac{S_6}{S_4} \rightarrow S_6 = \frac{g_{m6}}{g_{m4}} S_4$$

8. Calculate I_6 from

$$I_6 = \frac{g_{m6}^2}{2K'_6 S_6}$$

Check to make sure that S_6 satisfies the $V_{out}(\text{max})$ requirement and adjust as necessary.

9. Design S_7 to achieve the desired current ratios between I_5 and I_6 .

$$S_7 = (I_6/I_5)S_5 \quad (\text{Check the minimum output voltage requirements})$$

Unbuffered Op Amp Design Procedure - Continued

10. Check gain and power dissipation specifications.

$$A_v = \frac{2g_{m2}g_{m6}}{I_5(l_2 + l_4)I_6(l_6 + l_7)} \quad P_{diss} = (I_5 + I_6)(V_{DD} + |V_{SS}|)$$

11. If the gain specification is not met, then the currents, I_5 and I_6 , can be decreased or the W/L ratios of M2 and/or M6 increased. The previous calculations must be rechecked to insure that they are satisfied. If the power dissipation is too high, then one can only reduce the currents I_5 and I_6 . Reduction of currents will probably necessitate increase of some of the W/L ratios in order to satisfy input and output swings.

12. Simulate the circuit to check to see that all specifications are met.

DESIGN EXAMPLE OF A TWO-STAGE OP AMP

Example 230-1 - Design of a Two-Stage Op Amp

If $K_N' = 120 \mu\text{A}/\text{V}^2$, $K_P' = 25 \mu\text{A}/\text{V}^2$, $V_{TN} = |V_{TP}| = 0.5\text{V}$, $\lambda_N = 0.06\text{V}^{-1}$, and $\lambda_P = 0.08\text{V}^{-1}$, design a two-stage, CMOS op amp that meets the following specifications. Assume the channel length is to be $0.5 \mu\text{m}$ and the load capacitor is $C_L = 10\text{pF}$.

$$A_v > 3000\text{V/V} \quad V_{DD} = 2.5\text{V} \quad GB = 5\text{MHz} \quad SR > 10\text{V}/\mu\text{s}$$

$$60^\circ \text{ phase margin} \quad 0.5\text{V} < V_{out} \text{ range} < 2\text{V} \quad I_{CMR} = 1.25\text{V to } 2\text{V} \quad P_{diss} \leq 2\text{mW}$$

Solution

1.) The first step is to calculate the minimum value of the compensation capacitor C_c ,

$$C_c > (2.2/10)(10 \text{ pF}) = 2.2 \text{ pF}$$

2.) Choose C_c as 3pF . Using the slew-rate specification and C_c calculate I_5 .

$$I_5 = (3 \times 10^{-12})(10 \times 10^6) = 30 \mu\text{A}$$

3.) Next calculate $(W/L)_3$ using I_{CMR} requirements (use worst case thresholds $\pm 0.15\text{V}$).

$$(W/L)_3 = \frac{30 \times 10^{-6}}{(25 \times 10^{-6})[2.5 - 2 - .65 + 0.35]^2} = 30 \quad \rightarrow \quad \boxed{(W/L)_3 = (W/L)_4 = 30}$$

Example 230-1 - Continued

4.) Now we can check the value of the mirror pole, p_3 , to make sure that it is in fact greater than $10GB$. Assume the $C_{ox} = 6\text{fF}/\mu\text{m}^2$. The mirror pole can be found as

$$p_3 \approx \frac{-g_{m3}}{2C_{gs3}} = \frac{-\sqrt{2K'_p S_3 I_3}}{2(0.667)W_3 L_3 C_{ox}} = -1.25 \times 10^9 (\text{rads/sec})$$

or 199 MHz . Thus, p_3 , is not of concern in this design because $p_3 \gg 10GB$.

5.) The next step in the design is to calculate g_{m1} to get

$$g_{m1} = (5 \times 10^6)(2\pi)(3 \times 10^{-12}) = 94.25 \mu\text{S}$$

Therefore, $(W/L)_1$ is

$$(W/L)_1 = (W/L)_2 = \frac{g_{m1}^2}{2K'_N I_1} = \frac{(94.25)^2}{2 \cdot 120 \cdot 15} = 2.47 \approx 3.0 \Rightarrow \boxed{(W/L)_1 = (W/L)_2 = 3}$$

6.) Next calculate V_{DS5} ,

$$V_{DS5} = 1.25 - \sqrt{\frac{30 \times 10^{-6}}{120 \times 10^{-6} \cdot 3} - .65} = 0.31\text{V}$$

Using V_{DS5} calculate $(W/L)_5$ from the saturation relationship.


$$(W/L)_5 = \frac{2(30 \times 10^{-6})}{(120 \times 10^{-6})(0.31)^2} = 5.16 \approx 6 \quad \rightarrow \quad \boxed{(W/L)_5 = 6}$$

RIGHT-HALF PLANE ZERO

Controlling the Right-Half Plane Zero

Why is the RHP zero a problem?

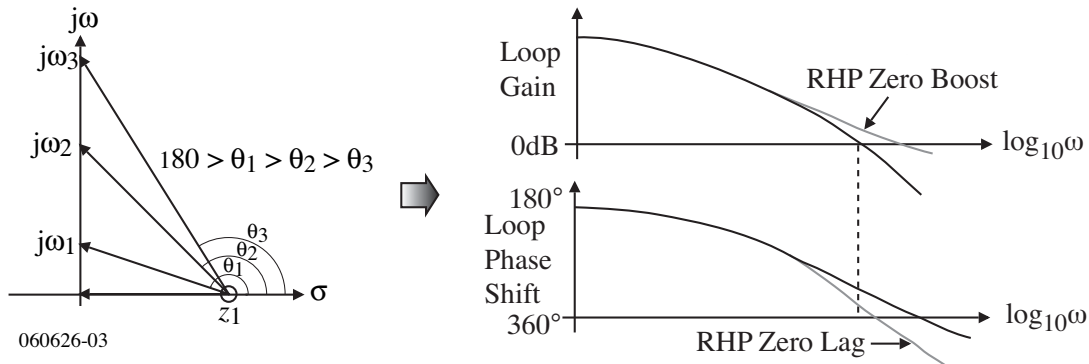Because it boosts the magnitude but lags the phase - the worst possible combination for stability.




Solution of the problem:

The compensation comes from the *feedback path* through C_C , but the RHP zero comes from the *feedforward path* through C_C so eliminate the feedforward path!

Use of Buffer to Eliminate the Feedforward Path through the Miller Capacitor

Model:

 The transfer function is given by the following equation,



$$\frac{V_o(s)}{V_{in}(s)} = \frac{(g_{mI})(g_{mII})(R_I)(R_{II})}{1 + s[R_IC_I + R_{II}C_{II} + R_IC_c + g_{mII}R_IR_{II}C_c] + s^2[R_IR_{II}C_{II}(C_I + C_c)]}$$

Using the technique as before to approximate p_1 and p_2 results in the following

$$p_1 \approx \frac{-1}{R_IC_I + R_{II}C_{II} + R_IC_c + g_{mII}R_IR_{II}C_c} \approx \frac{-1}{g_{mII}R_IR_{II}C_c}$$

and

$$p_2 \approx \frac{-g_{mII}C_c}{C_{II}(C_I + C_c)}$$

Comments:

Poles are approximately what they were before with the zero removed.

For 45° phase margin, $|p_2|$ must be greater than GB

For 60° phase margin, $|p_2|$ must be greater than $1.73GB$

Use of Buffer with Finite Output Resistance to Eliminate the RHP Zero

Assume that the unity-gain buffer has an output resistance of R_o .

Model:

 


Fig. 430-03

It can be shown that if the output resistance of the buffer amplifier, R_o , is not neglected that another pole occurs at,

$$p_4 \approx \frac{-1}{R_o[C_I C_c / (C_I + C_c)]}$$

and a LHP zero at

$$z_2 \approx \frac{-1}{R_o C_c}$$

Closer examination shows that if a resistor, called a *nulling resistor*, is placed in series with C_c that the RHP zero can be eliminated or moved to the LHP.

Use of Nulling Resistor to Eliminate the RHP Zero (or turn it into a LHP zero)[†]

 


Fig. 430-04

Nodal equations:

$$g_{mI}V_{in} + \frac{V_I}{R_I} + sC_I V_I + \left(\frac{sC_c}{1 + sC_c R_z} \right) (V_I - V_{out}) = 0$$

$$g_{mII}V_I + \frac{V_o}{R_{II}} + sC_{II}V_{out} + \left(\frac{sC_c}{1 + sC_c R_z} \right) (V_{out} - V_I) = 0$$

Solution:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{a\{1 - s[(C_c/g_{mII}) - R_z C_c]\}}{1 + bs + cs^2 + ds^3}$$

where

$$a = g_{mI}g_{mII}R_I R_{II}$$

$$b = (C_{II} + C_c)R_{II} + (C_I + C_c)R_I + g_{mII}R_I R_{II}C_c + R_z C_c$$

$$c = [R_I R_{II}(C_I C_{II} + C_c C_I + C_c C_{II}) + R_z C_c (R_I C_I + R_{II} C_{II})]$$

$$d = R_I R_{II} R_z C_I C_{II} C_c$$

[†] W.J. Parrish, "An Ion Implanted CMOS Amplifier for High Performance Active Filters", Ph.D. Dissertation, 1976, Univ. of CA., Santa Barbara.

Use of Nulling Resistor to Eliminate the RHP - Continued

If R_z is assumed to be less than R_I or R_{II} and the poles widely spaced, then the roots of the above transfer function can be approximated as

$$p_1 \approx \frac{-1}{(1 + g_{mII}R_{II})R_IC_c} \approx \frac{-1}{g_{mII}R_{II}R_IC_c}$$

$$p_2 \approx \frac{-g_{mII}C_c}{C_IC_{II} + C_cC_I + C_cC_{II}} \approx \frac{-g_{mII}}{C_{II}}$$

$$p_4 = \frac{-1}{R_zC_I}$$

and

$$z_1 = \frac{1}{C_c(1/g_{mII} - R_z)}$$

Note that the zero can be placed anywhere on the real axis.

A Design Procedure that Allows the RHP Zero to Cancel the Output Pole, p_2

We desire that $z_1 = p_2$ in terms of the previous notation.

Therefore,

$$\frac{1}{C_c(1/g_{mII} - R_z)} = \frac{-g_{mII}}{C_{II}}$$

The value of R_z can be found as

$$R_z = \left(\frac{C_c + C_{II}}{C_c} \right) (1/g_{mII})$$

 


Fig. 430-06

With p_2 canceled, the remaining roots are p_1 and p_4 (the pole due to R_z). For unity-gain stability, all that is required is that

$$|p_4| > A_v(0)|p_1| = \frac{A_v(0)}{g_{mII}R_{II}R_IC_c} = \frac{g_{mI}}{C_c}$$

and $(1/R_zC_I) > (g_{mI}/C_c) = GB$


Substituting R_z into the above inequality and assuming $C_{II} \gg C_c$ results in

$$C_c > \sqrt{\frac{g_{mI}}{g_{mII}}} C_IC_{II}$$

This procedure gives excellent stability for a fixed value of C_{II} ($\approx C_L$).

Unfortunately, as C_L changes, p_2 changes and the zero must be readjusted to cancel p_2 .

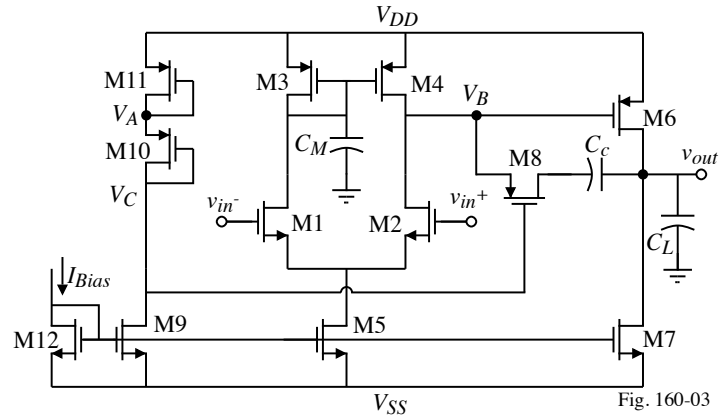Incorporating the Nulling Resistor into the Miller Compensated Two-Stage Op Amp Circuit:



We saw earlier that the roots were:

$$p_1 = -\frac{g_{m2}}{A_v C_c} = -\frac{g_{m1}}{A_v C_c} \quad p_2 = -\frac{g_{m6}}{C_L}$$

$$p_4 = -\frac{1}{R_z C_I} \quad z_1 = \frac{-1}{R_z C_c - C_c / g_{m6}}$$

where $A_v = g_{m1} g_{m6} R_I R_{II}$.

(Note that p_4 is the pole resulting from the nulling resistor compensation technique.)

Design of the Nulling Resistor (M8)

For the zero to be on top of the second pole (p_2), the following relationship must hold

$$R_z = \frac{1}{g_{m6}} \left(\frac{C_L + C_c}{C_c} \right) = \left(\frac{C_c + C_L}{C_c} \right) \frac{1}{\sqrt{2K'_p S_6 I_6}}$$

The resistor, R_z , is realized by the transistor M8 which is operating in the active region because the dc current through it is zero. Therefore, R_z can be written as

$$R_z = \left. \frac{\partial v_{DS8}}{\partial i_{D8}} \right|_{V_{DS8}=0} = \frac{1}{K'_p S_8 (V_{SG8} - |V_{TP}|)}$$

The bias circuit is designed so that voltage V_A is equal to V_B .

$$\therefore |V_{GS10}| - |V_T| = |V_{GS8}| - |V_T| \Rightarrow V_{SG11} = V_{SG6} \Rightarrow \left(\frac{W_{11}}{L_{11}} \right) = \left(\frac{I_{10}}{I_6} \right) \left(\frac{W_6}{L_6} \right)$$

In the saturation region

$$|V_{GS10}| - |V_T| = \sqrt{\frac{2(I_{10})}{K'_p (W_{10}/L_{10})}} = |V_{GS8}| - |V_T|$$

$$\therefore R_z = \frac{1}{K'_p S_8} \sqrt{\frac{K'_p S_{10}}{2I_{10}}} = \frac{1}{S_8} \sqrt{\frac{S_{10}}{2K'_p I_{10}}}$$

$$\text{Equating the two expressions for } R_z \text{ gives } \left(\frac{W_8}{L_8} \right) = \left(\frac{C_c}{C_L + C_c} \right) \sqrt{\frac{S_{10} S_6 I_6}{I_{10}}}$$

Example 230-2 - RHP Zero Compensation

Use results of Ex. 230-1 and design compensation circuitry so that the RHP zero is moved from the RHP to the LHP and placed on top of the output pole p_2 . Use device data given in Ex. 230-1.

Solution

The task at hand is the design of transistors M8, M9, M10, M11, and bias current I_{10} . The first step in this design is to establish the bias components. In order to set V_A equal to V_B , then V_{SG11} must equal V_{SG6} . Therefore,

$$S_{11} = (I_{11}/I_6)S_6$$


Choose $I_{11} = I_{10} = I_9 = 15\mu\text{A}$ which gives $S_{11} = (15\mu\text{A}/95\mu\text{A})190 = 30$.

The aspect ratio of M10 is essentially a free parameter, and will be set equal to 1. There must be sufficient supply voltage to support the sum of V_{SG11} , V_{SG10} , and V_{DS9} . The ratio of I_{10}/I_5 determines the (W/L) of M9. This ratio is

$$(W/L)_9 = (I_{10}/I_5)(W/L)_5 = (15/30)(6) = 3$$

Now $(W/L)_8$ is determined to be

$$(W/L)_8 = \left(\frac{3\text{pF}}{3\text{pF} + 10\text{pF}} \right) \sqrt{\frac{1 \cdot 190 \cdot 95\mu\text{A}}{15\mu\text{A}}} = 8$$

 

Example 230-2 - Continued

It is worthwhile to check that the RHP zero has been moved on top of p_2 . To do this, first calculate the value of R_z . V_{SG8} must first be determined. It is equal to V_{SG10} , which is

$$V_{SG10} = \sqrt{\frac{2I_{10}}{K'_p S_{10}}} + |V_{TP}| = \sqrt{\frac{2 \cdot 15}{25 \cdot 1}} + 0.5 = 1.595\text{V}$$

Next determine R_z .

$$R_z = \frac{1}{K'_p S_8 (V_{SG10} - |V_{TP}|)} = \frac{10^6}{25 \cdot 8 (1.595 - 0.7)} = 4.564\text{k}\Omega$$

The location of z_1 is calculated as

$$z_1 = \frac{-1}{(4.564 \times 10^3)(3 \times 10^{-12}) - \frac{3 \times 10^{-12}}{950 \times 10^{-6}}} = -94.91 \times 10^6 \text{ rads/sec}$$

The output pole, p_2 , is

$$p_2 = -\frac{950 \times 10^{-6}}{10 \times 10^{-12}} = -95 \times 10^6 \text{ rads/sec}$$

Thus, we see that for all practical purposes, the output pole is canceled by the zero that has been moved from the RHP to the LHP.

The results of this design are summarized below where $L = 0.5\mu\text{m}$.

$$W_8 = 4\mu\text{m} \quad W_9/L_9 = 1.5\mu\text{m} \quad W_{10} = 0.5\mu\text{m} \quad \text{and} \quad W_{11} = 15\mu\text{m}$$

An Alternate Form of Nulling Resistor

To cancel p_2 ,

$$z_1 = p_2 \rightarrow R_z = \frac{C_c + C_L}{g_{m6A} C_c} = \frac{1}{g_{m6B}}$$

Which gives

$$g_{m6B} = g_{m6A} \left(\frac{C_c}{C_c + C_L} \right)$$

In the previous example,

$$g_{m6A} = 950 \mu\text{S}, C_c = 3 \text{ pF}$$

and $C_L = 10 \text{ pF}$.

Choose $I_{6B} = 10 \mu\text{A}$ to get

$$g_{m6B} = \frac{g_{m6A} C_c}{C_c + C_L} \rightarrow \sqrt{\frac{2K_P W_{6B} I_{6B}}{L_{6B}}} = \left(\frac{C_c}{C_c + C_L} \right) \sqrt{\frac{2K_P W_{6A} I_{6A}}{L_{6A}}}$$

or

$$\frac{W_{6B}}{L_{6B}} = \left(\frac{3}{13} \right)^2 \frac{I_{6A}}{I_{6B}} \frac{W_{6A}}{L_{6A}} = \left(\frac{3}{13} \right)^2 \left(\frac{95}{10} \right) (190) = 96.12 \rightarrow W_{6B} = 48 \mu\text{m}$$

 


Fig. 6.3-4A

Increasing the Magnitude of the Output Pole[†]

The magnitude of the output pole, p_2 , can be increased by introducing gain in the Miller capacitor feedback path. For example,

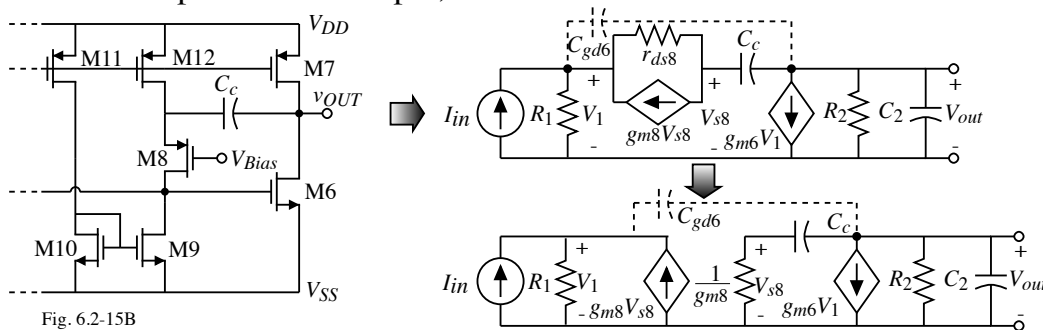


Fig. 6.2-15B

The resistors R_1 and R_2 are defined as

$$R_1 = \frac{1}{g_{ds2} + g_{ds4} + g_{ds9}} \quad \text{and} \quad R_2 = \frac{1}{g_{ds6} + g_{ds7}}$$

where transistors M2 and M4 are the output transistors of the first stage.

Nodal equations:

$$I_{in} = G_1 V_1 - g_{m8} V_{s8} = G_1 V_1 - \left(\frac{g_{m8} s C_c}{g_{m8} + s C_c} \right) V_{out} \quad \text{and} \quad 0 = g_{m6} V_1 + \left[G_2 + s C_2 + \frac{g_{m8} s C_c}{g_{m8} + s C_c} \right] V_{out}$$

[†] B.K. Ahuja, "An Improved Frequency Compensation Technique for CMOS Operational Amplifiers," *IEEE J. of Solid-State Circuits*, Vol. SC-18, No. 6 (Dec. 1983) pp. 629-633.

Increasing the Magnitude of the Output Pole - Continued

Solving for the transfer function V_{out}/I_{in} gives,

$$\frac{V_{out}}{I_{in}} = \left(\frac{-g_{m6}}{G_1 G_2} \right) \left[\frac{\left(1 + \frac{sC_c}{g_{m8}} \right)}{1 + s \left[\frac{C_c}{g_{m8}} + \frac{C_2}{G_2} + \frac{C_c}{G_2} + \frac{g_{m6}C_c}{G_1 G_2} \right] + s^2 \left(\frac{C_c C_2}{g_{m8} G_2} \right)} \right]$$

Using the approximate method of solving for the roots of the denominator gives

$$p_1 = \frac{-1}{\frac{C_c}{g_{m8}} + \frac{C_c}{G_2} + \frac{C_2}{G_2} + \frac{g_{m6}C_c}{G_1 G_2}} \approx \frac{-6}{g_{m6}r_{ds}^2 C_c}$$

$$\text{and } p_2 \approx \frac{-\frac{g_{m6}r_{ds}^2 C_c}{6}}{\frac{C_c C_2}{g_{m8} G_2}} = \frac{g_{m8}r_{ds}^2 G_2}{6} \left(\frac{g_{m6}}{C_2} \right) = \left(\frac{g_{m8}r_{ds}}{3} \right) |p_2'|$$

where all the various channel resistance have been assumed to equal r_{ds} and p_2' is the output pole for normal Miller compensation.


Result:

Dominant pole is approximately the same and the output pole is increased by $\approx g_{m8}r_{ds}$.

Increasing the Magnitude of the Output Pole - Continued

In addition there is a LHP zero at $-g_{m8}/sC_c$ and a RHP zero due to C_{gd6} (shown dashed in the previous model) at g_{m6}/C_{gd6} .

Roots are:

 


Concept:

$$R_{out} = r_{ds7} \parallel \left(\frac{3}{g_{m6}g_{m8}r_{ds8}} \right) \approx \frac{3}{g_{m6}g_{m8}r_{ds8}}$$

Therefore, the output pole is approximately,

$$|p_2| \approx \frac{g_{m6}g_{m8}r_{ds8}}{3C_{II}}$$

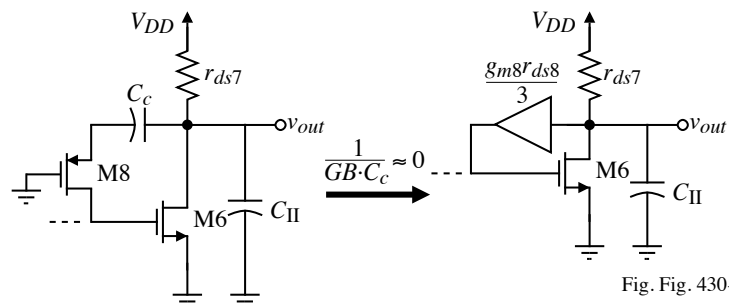



POWER SUPPLY REJECTION RATIO OF THE TWO-STAGE OP AMP

What is *PSRR*?

$$PSRR = \frac{A_v(V_{dd}=0)}{A_{dd}(V_{in}=0)}$$

How do you calculate *PSRR*?

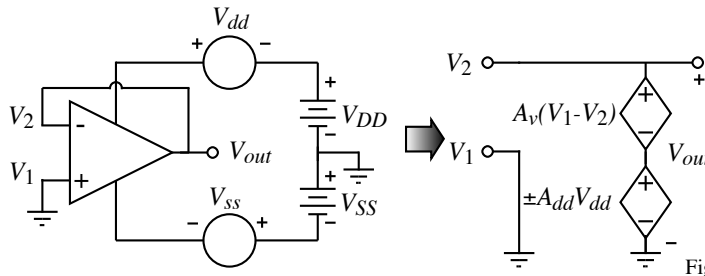 
You could calculate A_v and A_{dd} and divide, however



$$V_{out} = A_{dd}V_{dd} + A_v(V_1 - V_2) = A_{dd}V_{dd} - A_vV_{out} \rightarrow V_{out}(1 + A_v) = A_{dd}V_{dd}$$

$$\therefore \frac{V_{out}}{V_{dd}} = \frac{A_{dd}}{1 + A_v} \approx \frac{A_{dd}}{A_v} = \frac{1}{PSRR+} \quad (\text{Good for frequencies up to } GB)$$

Approximate Model for *PSRR+*

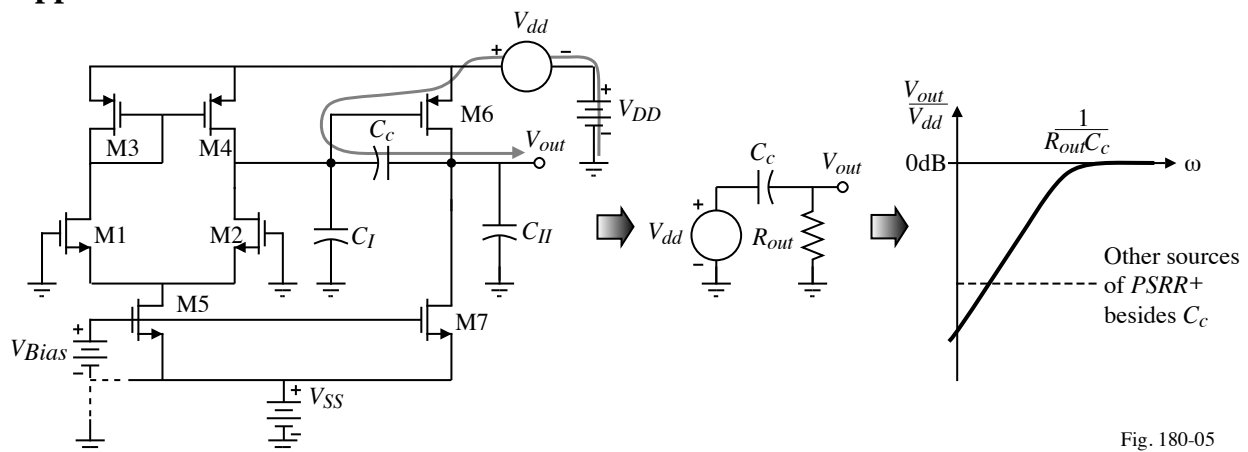

- 1.) The M7 current sink causes V_{SG6} to act like a battery.
- 2.) Therefore, V_{dd} couples from the source to gate of M6.
- 3.) The path to the output is through any capacitance from gate to drain of M6.

Conclusion:

The Miller capacitor C_c couples the positive power supply ripple directly to the output.
Must reduce or eliminate C_c .

Approximate Model for $PSRR^-$

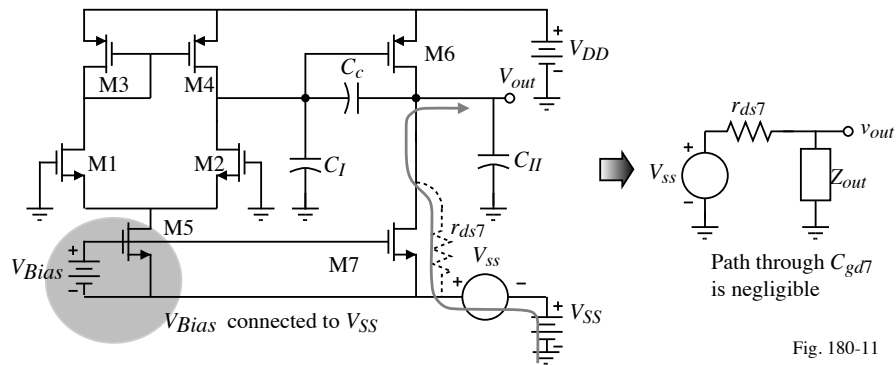


Fig. 180-11

What is Z_{out} ?

$$Z_{out} = \frac{V_t}{I_t} \Rightarrow I_t = g_{mII} V_1 = g_{mII} \left(\frac{g_{mI} V_t}{G_I + sC_I + sC_C} \right)$$

$$\text{Thus, } Z_{out} = \frac{G_I + s(C_I + C_C)}{g_{mI} g_{mII}}$$

\therefore

 


Fig.180-12

$$\frac{V_{out}}{V_{ss}} = \frac{1 + \frac{r_{ds7}}{Z_{out}}}{1} = \frac{s(C_C + C_I) + G_I + g_{mI} g_{mII} r_{ds7}}{s(C_C + C_I) + G_I} \Rightarrow \text{Pole at } \frac{-G_I}{C_C + C_I}$$

The negative $PSRR$ is much better than the positive $PSRR$.

CMOS Analog Circuit Design

© P.E. Allen - 2010

SUMMARY

- The output of the design of an op amp is
 - Schematic
 - DC currents
 - W/L ratios
 - Component values
- Design procedures provide an organized approach to creating the dc currents, W/L ratios, and the component values
- The right-half plane zero causes the Miller compensation to deteriorate
- Methods for eliminating the influence of the RHP zero are:
 - Nulling resistor
 - Increasing the magnitude of the output pole
- The $PSRR$ of the two-stage op amp is poor because of the Miller capacitance, however, methods exist to eliminate this problem
- The two-stage op amp is a very general and flexible op amp